 


Boolean Algebra and Sequential Logic

Digital Circuits: Two voltage levels

- High/true/1/asserted
- Low/false/0/deasserted



Advantages of digital circuits over analog circuits

- More reliable (simpler circuits, less noise-prone)
- Specified accuracy (determinable)
- Abstraction can be applied using simple mathematical model
- Ease design, analysis and simplification of digital circuit

Precedence of Operators: Not (') > And (·) > Or (+)

Laws of Boolean Algebra

Identity laws

$$A + 0 = 0 + A = A \quad A \cdot 1 = 1 \cdot A = A$$

Inverse/complement laws

$$A + A' = A' + A = 1 \quad A \cdot A' = A' \cdot A = 0$$

Commutative laws

$$A + B = B + A \quad A \cdot B = B \cdot A$$

Associative laws *

$$A + (B + C) = (A + B) + C \quad A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

Distributive laws

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C) \quad A + (B \cdot C) = (A + B) \cdot (A + C)$$

Idempotency

$$X + X = X \quad X \cdot X = X$$

One element / Zero element

$$X + 1 = 1 + X = 1 \quad X \cdot 0 = 0 \cdot X = 0$$

Involution

$$(X')' = X$$

Absorption 1

$$X + X \cdot Y = X \quad X \cdot (X + Y) = X$$

Absorption 2

$$X + X' \cdot Y = X + Y \quad X \cdot (X' + Y) = X' \cdot Y$$

De Morgans' (can be generalised to more than 2 variables)

$$(X + Y)' = X' \cdot Y' \quad (X \cdot Y)' = X' + Y'$$

Consensus

$$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z \quad (X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$$

Duality

- **duality** → if the AND/OR operators and identity elements 0/1 are interchanged in a boolean equation, it remains valid
- e.g. the dual equation of $a + (b \cdot c) = (a + b) \cdot (a + c)$ is $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
- e.g. if $x + 1 = 1$ is valid, then its dual $x \cdot 0 = 0$ is also valid.

Function

- boolean functions: e.g. $F1(x, y, z) = x \cdot y \cdot z'$
 - to prove that $F1 = F2$: use truth table
- **complement function** → given boolean function F , the complement of F , denoted F' , is obtained by interchanging 1 with 0 in the function's output values.

Standard Forms: Every Boolean expression can be expressed in SOP or POS form.

- Sum-of-Products (SOP)
- Product-of-Sums (POS)

Literals: A Boolean var. on its **own** or in its **complemented** form, i.e. x, x', y, y'

Product term: A single literal or a logical product (**AND**) of several literals

Examples: (1) x , (2) $x \cdot y \cdot z'$, (3) $A' \cdot B$, (4) $A \cdot B$, (5) $d \cdot g' \cdot v \cdot w$

Sum term: A single literal or a logical sum of several literals

Examples: (1) x , (2) $x + y + z'$, (3) $A' + B$, (4) $A + B$

SOP expression: A product term or a logical sum of several product terms

Examples: (1) x , (2) $x + y \cdot z'$, (3) $x \cdot y' + x' \cdot y \cdot z$, (4) $A \cdot B + A' \cdot B'$

POS expression: A sum term or a logical product (**AND**) of several sum terms

Examples: (1) x , (2) $x \cdot (y + z')$, (3) $(x + y') \cdot (x' + y + z)$

Conversion

$$F(x, y, z) = \Sigma m(1, 4, 5, 6, 7) = \Pi M(0, 2, 3)$$

In truth table: $F' = m0 + m2 + m3$

Therefore

$$F = (m0 + m2 + m3)' = m0' \cdot m2' \cdot m3' \\ = M0 \cdot M2 \cdot M3$$

Minterm and Maxterm: In general, with n variables we have up to 2^n minterms and 2^n maxterms.

Minterm of n variables is a product term that contains n literals from **all** the variables.

Example: On 2 variables x and y , the minterms are: $x' \cdot y'$, $x' \cdot y$, $x \cdot y'$ and $x \cdot y$

Maxterm of n variables is a sum term that contains n literals from **all** the variables.

Example: On 2 variables x and y , the maxterms are: $x' + y'$, $x' + y$, $x + y'$ and $x + y$

x	y	Minterms		Maxterms	
		Term	Notation	Term	Notation
0	0	$x' \cdot y'$	m0	$x + y$	M0
0	1	$x' \cdot y$	m1	$x + y'$	M1
1	0	$x \cdot y'$	m2	$x' + y$	M2
1	1	$x \cdot y$	m3	$x' + y'$	M3

Min: NOT=0

Max: NOT=1

Canonical/normal form: a unique form of representation.


- Sum-of-minterms = Canonical sum-of-products
- Product-of-maxterms = Canonical product-of-sums

Gray Code

- Unweighted (not an arithmetic code)
- Only a single bit change from one code value to the next.
- Not restricted to decimal digits: n bits $\Rightarrow 2^n$ values.
- Good for error detection.

Decimal	Binary	Gray Code	Decimal	Binary	Gray code
0	0000	0000	8	1000	1100
1	0001	0001	9	1001	1101
2	0010	0011	10	1010	1111
3	0011	0010	11	1011	1110
4	0100	0110	12	1100	1010
5	0101	0111	13	1101	1011
6	0110	0101	14	1110	1001
7	0111	0100	15	1111	1000

Generate Gray Code

 


K-Map

- Each cell in n -variable K-map has n adjacent neighbours
- Arrangement ensures that minterms of adjacent cells differ by only *ONE literal*. [Gray Code]
- There is wrap-around in the K-map
- We can use K-map to simplify SOP and POS expression

Group: each valid grouping of adjacent cells containing '1' corresponds to a simpler product term

 - group must have size in powers of 2
- grouping 2^n adjacent cells **eliminates** n variables
- Select as few groups as possible to cover all the cells (minterms) of the function



Implicant: a product term that could be used to cover minterms of the function

Prime implicant (PI): a product term obtained by combining the *maximum possible number of minterms* from adjacent squares in the map. (biggest grouping possible.)

- Note: Group consist of only X is not considered as PI

Essential prime implicant (EPI): a prime implicant that includes at least one minterm that is not covered by any other prime implicant.

Don't-care conditions: In certain problems, some outputs are not specified or are invalid. Hence, these outputs can be either '1' or '0' \Rightarrow could be chosen to be either '1' or '0', depending on which choice results in a simpler expression.

- When select EPIs, if **all** the "not covered minterm" in the EPI are don't care condition, then we will **not** select it.


Tips

- larger group \Leftrightarrow fewer literals in the resulting product term
- fewer groups \Leftrightarrow fewer product terms in simplified SOP expression

Finding Simplified POS Expression

Simplified **POS** expression can be obtained by grouping the maxterms (i.e. 0s) of the given function.


$$F = \Sigma m(0,1,2,3,5,7,8,9,10,11)$$

 

$$F' = B \cdot D' + A \cdot B$$

$$F = (B \cdot D' + A \cdot B)' = (B \cdot D')' \cdot (A \cdot B)' = (B' + D) \cdot (A' + B')$$

Two classes of logic circuits

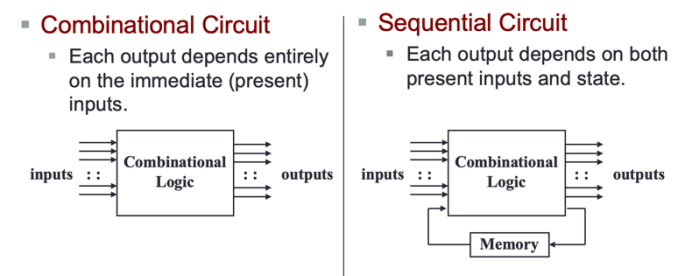


Memory element: a device which can remember value indefinitely, or change value on command from its inputs.

Command (at time t)	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1

$Q(t)$ or Q : current state
 $Q(t+1)$ or Q^* : next state

Two types of triggering/activation

 
- Pulse-triggered
 - Latches
 - ON = 1, OFF = 0




- Edge-triggered
 - Flip-flops
 - Positive edge-triggered (ON = from 0 to 1; OFF = other time)
 - Negative edge-triggered (ON = from 1 to 0; OFF = other time)

S-R Latch


R	S	$Q(t+1) = S + R' \cdot Q$
High	Low	Low (Reset)
Low	High	High (Set)
Low	Low	$Q(t)$ No change
High	High	Invalid, Outputs Q and Q' are both LOW

 

 Gated S-R Latch: S-R latch + enable input (EN) and 2 NAND gates → gated S-R latch. (Outputs change when EN is high)



Gated D Latch: Changes when EN is high

 

EN	D	$Q(t+1) = D$
High (1)	High (1)	Low (0) Reset
High (1)	Low (0)	High (1) Set
Low (0)	X	$Q(t)$ No change


Flip-flops: synchronous bistable devices.

- Output changes state at a specified point on a triggering input called the **clock**.
- Change state either at the **positive (rising) edge**, or at the **negative (falling) edge** of the clock signal.

S-R flip-flop: On the triggering edge of the clock pulse


D flip-flop: Single input D (data). On the triggering edge of the clock pulse

 J-K flip-flop: Q and Q' are fed back to the pulse-steering NAND gates. [No invalid state]



J	K	$Q(t+1) = J \cdot Q' + K' \cdot Q$
High	Low	High (Set)
Low	High	Low (Reset)
Low	Low	$Q(t)$ No change
High	High	$Q(t)'$ [Toggle]

 T flip-flop: Single input version of the J-K flip-flop, formed by tying both inputs together.




T	$Q(t+1) = T \cdot Q' + T' \cdot Q$
Low	$Q(t)$ No change
High	$Q(t)'$ [Toggle]

Asynchronous Inputs: S-R, D and J-K inputs are **synchronous** inputs, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.

- Affect the state of the flip-flop independent of the clock; example: *preset (PRE)* and *clear (CLR)* [or *direct set (SD)* and *direct reset (RD)*].
- When $PRE=HIGH$, Q is immediately set to HIGH.
- When $CLR=HIGH$, Q is immediately cleared to LOW.
- Flip-flop in normal operation mode when both PRE and CLR are LOW.


[Example] A J-K flip-flop with active-low PRESET and CLEAR asynchronous inputs.

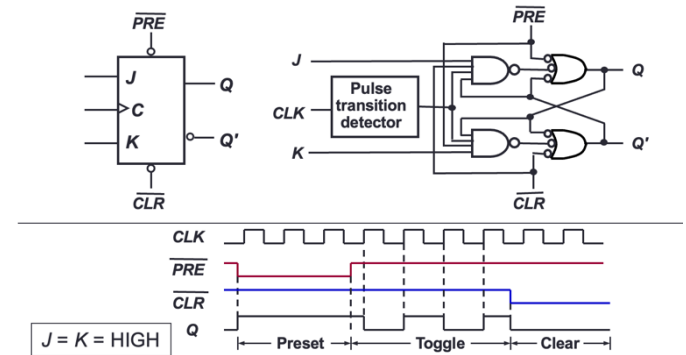**Sequential Circuit Analysis [Characteristic tables]**

State Table: m flip-flops and n inputs → 2^{m+n} rows.

State diagram: m flip-flops → up to 2^m states

- Each state is denoted by a circle.
- Each arrow denotes a **transition** of the sequential circuit
- A label of the form a/b is attached to each arrow where a (if there is one) denotes the **inputs** while b (if there is one) denotes the **outputs** of the circuit in that transition. [Input/Output]

 **Concept**


- A state is called a **sink** if once the circuit enters this state, it never moves out of that state
- A circuit is **self-correcting** if for some reason the circuit enters into any unused (invalid) state, it is able to transit to a valid state after a finite number of transitions.

Sequential Circuit Design [Excitation tables]

- Description of circuit behavior [state diagram/ table]
- Derive the state table.
- Perform state reduction if necessary.
- Perform state assignment.
- Determine number of flip-flops and label them.
- Choose the type of flip-flop to be used.
- Derive circuit excitation and output tables from state table
- Derive circuit output functions and flip-flop input functions.
- Draw the logic diagram.

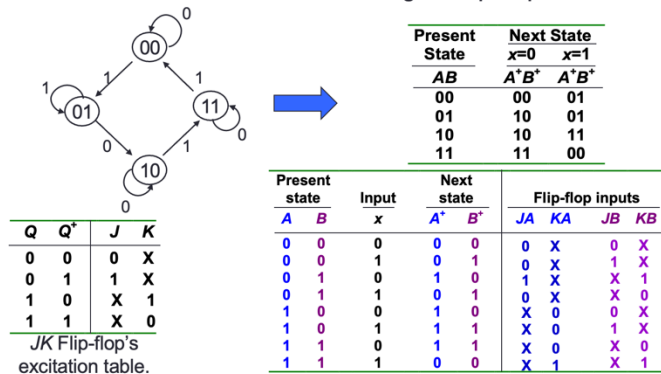
[Example]

- Circuit state/excitation table, using JK flip-flops.



Derive Flip-flop input functions

- $JA = B \cdot x'$
- $JB = x$
- $KA = B \cdot x$
- $KB = (A \oplus x)'$

 **Flip-flop Characteristic Tables**

J	K	Q(t+1)	Comments
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q(t)'	Toggle

S	R	Q(t+1)	Comments
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

D	Q(t+1)
0	0
1	1

T	Q(t+1)
0	Q(t)
1	Q(t)'

Flip-flop Excitation Tables

Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop

Q	Q ⁺	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR Flip-flop

Q	Q ⁺	D
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-flop

Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0

T Flip-flop